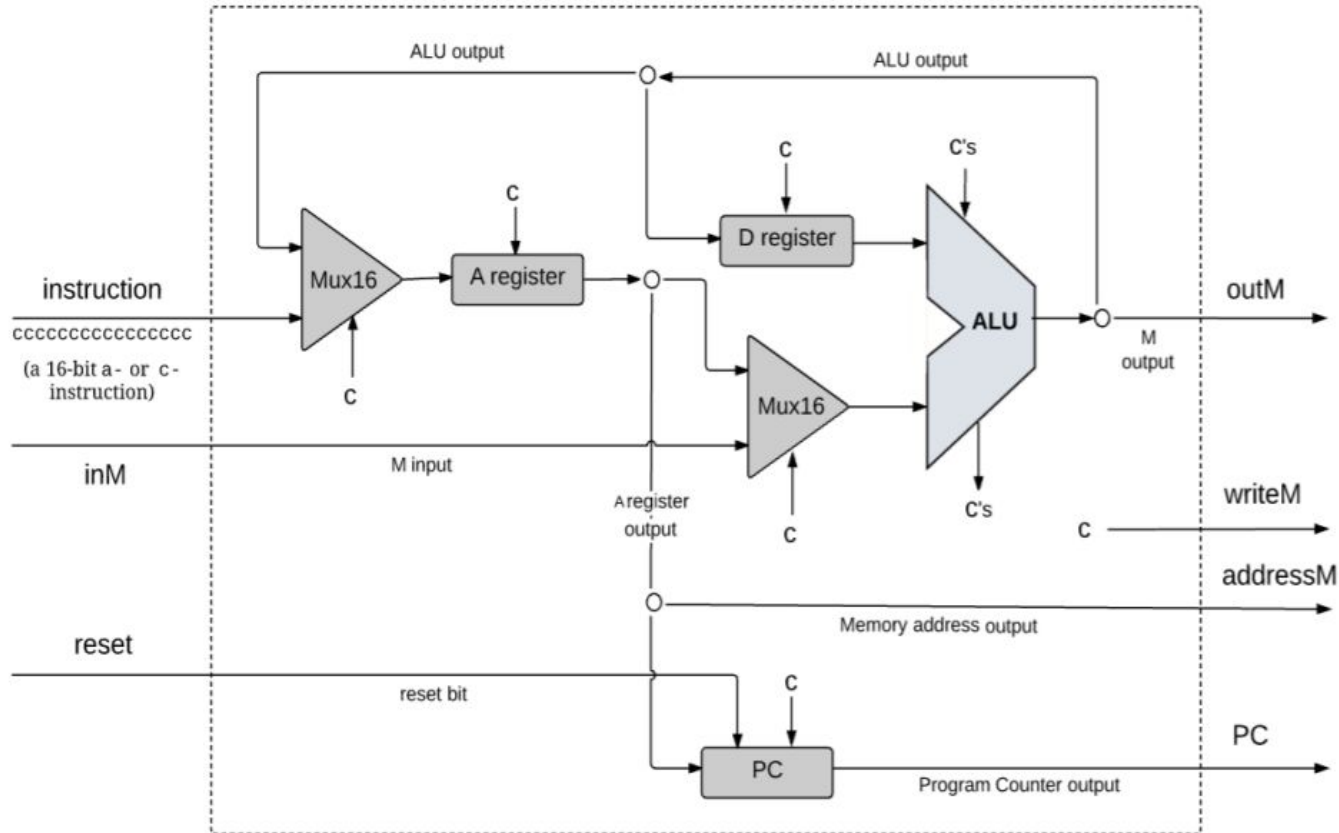


# ELEMENTS OF COMPUTING SYSTEM-1

# **Part A**

## Building of HACK CPU

# Block Diagram



# OUTPUT

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetrts\projects\05\CPU.hdl

File View Run Help

Chip Name: CPU (Clocked) Time: 0

Input pins		Output pins	
Name	Value	Name	Value
inM[16]	0	outM[16]	0
instruction[16]	0	writeM	0
reset	0	addressM[15]	0
		pc[15]	0

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press
// File name: projects/05/CPU.hdl
/*
 * The Hack Central Processing Unit
 * Parses the binary code in the instructionC
 * Hack machine language specification
 * function specified by the instructionC
 * value, the inM input is expected to write a value to the memory
 * output to the target address,
 * value may appear in outM.
 * If the reset input is 0, compare
 */
```

Internal pins	
Name	Value
instructionC	0
inA[16]	0
loadA	0
instCAndDestA	0
loadA	0
outA[16]	0
inD[16]	0
outD[16]	0
aluInY[16]	0
zrALU	1
ngALU	0

A: 0 D: 0 PC: 0

ALU

D Input: 0

M/A Input: 0

AND

ALU output: 0

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetrts\projects\05\CPU.hdl

File View Run Help

Chip Name: CPU (Clocked) Time: 46

Input pins		Output pins	
Name	Value	Name	Value
inM[16]	11111	outM[16]	1
instruction[16]	32767	writeM	1
reset	0	addressM[15]	32767
		pc[15]	0

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press
// File name: projects/05/CPU.hdl
/*
 * The Hack Central Processing Unit
 * Parses the binary code in the instructionC
 * Hack machine language specification
 * function specified by the instructionC
 * value, the inM input is expected to write a value to the memory
 * output to the target address,
 * value may appear in outM.
 * If the reset input is 0, compare
 */
```

Internal pins	
Name	Value
instructionC	0
inA[16]	0
loadA	0
instCAndDestA	0
loadA	0
outA[16]	0
inD[16]	0
outD[16]	0
aluInY[16]	0
zrALU	0
ngALU	0

End of script - Comparison ended successfully

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetrts\projects\05\CPU.hdl

File View Run Help

Chip Name: CPU (Clocked) Time: 46


Input pins		Output pins	
Name	Value	Name	Value
inM[16]	11111	outM[16]	1
instruction[16]	32767	writeM	1
reset	0	addressM[15]	32767
		pc[15]	0

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press
// File name: projects/05/CPU.hdl
/*
 * The Hack Central Processing Unit
 * Parses the binary code in the instructionC
 * Hack machine language specification
 * function specified by the instructionC
 * value, the inM input is expected to write a value to the memory
 * output to the target address,
 * value may appear in outM.
 * If the reset input is 0, compare
 */
```

Internal pins	
Name	Value
instructionC	0
inA[16]	0
loadA	0
instCAndDestA	0
loadA	0
outA[16]	0
inD[16]	0
outD[16]	0
aluInY[16]	0
zrALU	0
ngALU	0

End of script - Comparison ended successfully
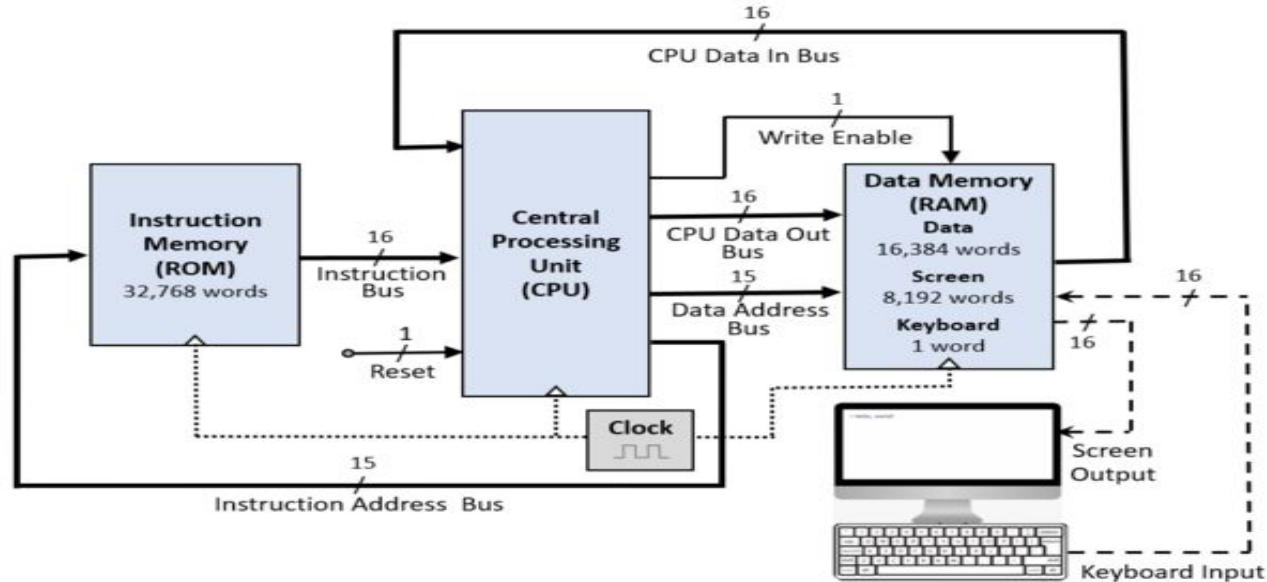
# Additional Development -Using CPU in Computer



# Output

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetr/projects\05\Computer.hdl

File View Run Help

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetr/projects\05\Computer.hdl

File View Run Help

Chip Name: **Computer (Clocked)** Time: **0**

**Input pins**

Name	Value
reset	0

**Output pins**

Name	Value
------	-------

**HDL**

```
// This file is part of www.nand2tetr.com
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press
// File name: projects/05/Computer.hdl
/*
 * The HACK computer, consisting of:
 * - When reset is 0, the program starts.
 * - When reset is 1, the program starts.
 * - Thus, to start running the program, set reset to 1, and then set reset to 0.
 * - From this point onwards, the program may show some output on the screen.
 * - Depending on the program's output, some input using the keyboard may be required.
 */
```

**Internal pins**

Name	Value
romAddress[15]	0
cpuInstruction[15]	0
cpuIn[16]	0
inMemory[16]	0
loadMemory	0
addressMemory...	0

**RAM 16K:**

Address	Value
0	0
1	0
2	0
3	0
4	0
5	0
6	0

**ROM: Asm**

Address	Value
0	00
1	00
2	00
3	00
4	00
5	00
6	00

**ALU**

D Input: 0

M/A Input: 0

ALU output: 0

**D&M**

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetr/projects\05\Computer.hdl

File View Run Help

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetr/projects\05\Computer.hdl

File View Run Help

Chip Name: **Computer (Clocked)** Time: **13**

**Input pins**

Name	Value
reset	0

**Output pins**

Name	Value
------	-------

**HDL**

```
// This file is part of www.nand2tetr.com
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press
// File name: projects/05/Computer.hdl
/*
 * The HACK computer, consisting of:
 * - When reset is 0, the program starts.
 * - When reset is 1, the program starts.
 * - Thus, to start running the program, set reset to 1, and then set reset to 0.
 * - From this point onwards, the program may show some output on the screen.
 * - Depending on the program's output, some input using the keyboard may be required.
 */
```

**Internal pins**

Name	Value
romAddress[15]	0
cpuInstruction[15]	0
cpuIn[16]	0
inMemory[16]	0
loadMemory	0
addressMemory...	0

**Time: 13**

Time	reset	romAddress[15]	cpuInstruction[15]	cpuIn[16]	inMemory[16]	loadMemory	addressMemory...
0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0
2	0	0	0	0	0	0	0
3	0	0	0	0	0	0	0
4	0	0	0	0	0	0	0
5	0	0	0	0	0	0	0
6	0	0	0	0	0	0	0
7	0	0	0	0	0	0	0
8	0	0	0	0	0	0	0
9	0	0	0	0	0	0	0
10	0	0	0	0	0	0	0
11	0	0	0	0	0	0	0
12	0	0	0	0	0	0	0
13	0	0	0	0	0	0	0

End of script - Comparison ended successfully

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetr/projects\05\Computer.hdl

File View Run Help

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\nand2tetr/projects\05\Computer.hdl

File View Run Help

Chip Name: **Computer (Clocked)** Time: **25**

**Input pins**

Name	Value
reset	0

**Output pins**

Name	Value
------	-------

**HDL**

```
// This file is part of www.nand2tetr.com
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press
// File name: projects/05/Computer.hdl
/*
 * The HACK computer, consisting of:
 * - When reset is 0, the program starts.
 * - When reset is 1, the program starts.
 * - Thus, to start running the program, set reset to 1, and then set reset to 0.
 * - From this point onwards, the program may show some output on the screen.
 * - Depending on the program's output, some input using the keyboard may be required.
 */
```

**Internal pins**

Name	Value
romAddress[15]	14
cpuInstruction[15]	14
cpuIn[16]	23456
inMemory[16]	0
loadMemory	0
addressMemory...	0

**Time: 25**

Time	reset	romAddress[15]	cpuInstruction[15]	cpuIn[16]	inMemory[16]	loadMemory	addressMemory...
0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0
2	0	0	0	0	0	0	0
3	0	0	0	0	0	0	0
4	0	0	0	0	0	0	0
5	0	0	0	0	0	0	0
6	0	0	0	0	0	0	0
7	0	0	0	0	0	0	0
8	0	0	0	0	0	0	0
9	0	0	0	0	0	0	0
10	0	0	0	0	0	0	0
11	0	0	0	0	0	0	0
12	0	0	0	0	0	0	0
13	0	0	0	0	0	0	0
14	0	0	0	0	0	0	0
15	0	0	0	0	0	0	0
16	0	0	0	0	0	0	0
17	0	0	0	0	0	0	0
18	0	0	0	0	0	0	0
19	0	0	0	0	0	0	0
20	0	0	0	0	0	0	0
21	0	0	0	0	0	0	0
22	0	0	0	0	0	0	0
23	0	0	0	0	0	0	0
24	0	0	0	0	0	0	0
25	0	0	0	0	0	0	0

End of script - Comparison ended successfully

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\yand2tetris\projects\05\Computer.hdl

File View Run Help

Animate Program flow Format: Decimal View: Screen

Chip Name: Computer (Clocked) Time: 63

Input pins

Name	Value
reset	0

Output pins

Name	Value
score	0

HDL

```

* set reset to 1, and then set
* From this point onwards, the
* Depending on the program's or
* the screen may show some out
* some input using the keyboard
*/
CHIP Computer {
  IN reset;

  PARTS:
    ROM16K(address=romAddress, c
    CPU16K(address=romAddress, c
    Memory16K(address=romAddress, load=lo
  }
  
```

Internal pins

Name	Value
romAddress[15]	24
cpuInstruction...	-5497
cpuIn[16]	0
loadMemory[16]	0
loadMemory	0
addressMemory...	23

RAM 16K:

Address	Value
20	0
21	0
22	0
23	0
24	0
25	0
26	0

ROM: 16K

Address	Value
18	111001100001000
19	000000000010000
20	111111001001000
21	000000000001000
22	111000110000000
23	000000000010111
24	1110101010000111

ALU

D Input: 0

W/A Input: 23

ALU output: 0

End of script - Comparison ended successfully

Hardware Simulator (2.5) - C:\Users\nehar\Desktop\resources\yand2tetris\projects\05\Computer.hdl

File View Run Help

Animate Program flow Format: Decimal View: Screen

Chip Name: Computer (Clocked) Time: 0

Input pins

Name	Value
reset	0

Output pins

Name	Value
score	0

HDL

```

* set reset to 1, and then set
* From this point onwards, the
* Depending on the program's or
* the screen may show some out
* some input using the keyboard
*/
CHIP Computer {
  IN reset;

  PARTS:
    ROM16K(address=romAddress, c
    CPU16K(address=romAddress, c
    Memory16K(address=romAddress, load=lo
  }
  
```

Internal pins

Name	Value
romAddress[15]	0
cpuInstruction...	0
cpuIn[16]	0
loadMemory[16]	0
loadMemory	0
addressMemory...	0

RAM 16K:

Address	Value
205	0
206	0
207	0
208	0
209	0
210	0
211	0

ROM: 16K

Address	Value
18	0
19	0
20	0
21	0
22	0
23	0
24	0

ALU

D Input: 0

W/A Input: 0

ALU output: 0

## **Part B**

Design and implement a digital system that takes the Gray code output from a rotary encoder and displays the rotary shaft position on a 7-segment display




# What a Rotary Encoder is ?

- Definition: Rotary encoders are electromechanical devices used to convert the angular position of a shaft into an electrical signal.
- Commonly used in various applications for measuring rotation and angular displacement.
- Utilizes optical or magnetic sensors to detect changes in position.
- Optical encoders use light and a patterned disc, while magnetic encoders use a magnetized disc and sensors.



# What is a 7 Segment display ?

 

Seven segment display is an electric component that consists of seven individual LEDs arranged in the form of the number 8 labeled from a to g. The primary function of the seven segment display is to visually represent the decimal numbers from 0 to 9 by illuminating the seven segments.

# Proposed project

- Converting Gray Code output of Rotary encoder to display shafts position to display the shaft's position in a 7 segment display
- Involves 3 basic steps which involves various conversions, which is gray to binary, binary to decimal, decimal to 7 segment display
- Function can be amplified using a microcontroller
- Rigorous testing and further debugging crucial to know its feasibility
- Involves usage of Logic gates for a huge portion

Consider each digit of Gray code as A,B,C,D respectively


A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	1	1	1	0	1	1	0	1
0	0	1	0	1	1	1	1	0	0	1
0	1	1	0	0	1	1	0	0	1	1
0	1	1	1	1	0	1	1	0	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	0	0	1	1	1	0	0	0	0
1	1	0	0	1	1	1	1	1	1	1
1	1	0	1	1	1	1	1	0	1	1

ABCD	00	01	11	10
00	1	0	1	1
01	1	1	1	0
11	1	1	X	X
10	X	X	X	X

Involves the usage of multiple k-maps

This can be obtained by the standard algorithm for its solution involving isolation of even number of ones to the maximum extent possible

 The above example is for first line of gray code which is being converted to binary



# Application of Logic Gates


Logic gates can be utilized to interpret the outcomes from Kmaps to understand whole thing easier

The above is logic gate for kmap given in previous slide

For segment 'a'

The three major lines represent B,C,D


$$a = BC' + B'D' + CD$$

 

For segment 'c'.

The three major lines represents B,C,D.


$$c = C' + D' + B$$

 

For segment 'b'

The three major lines represents A,B,D


$$b = C' + D' + B$$

 

**For segment 'd'**

The three major lines represent A,B,C,D.


$$d = A + BD + CD + B'D'$$

 

**For segment 'e':**

The four major lines are A,B,C,D


$$e = A'BC'D + AD' + BCD + B'C'D'$$

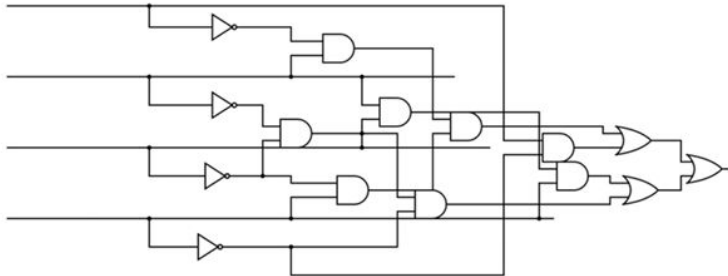

**For segment 'f'**

The major lines are A,B,C,D.


$$f = BD + BC + A + B'C'D$$

 

**For segment 'g'**

The major lines are A,B,C,D

$$g = BD + A + C$$

 



# Generating the output

The following three  
Are the output  
pages

Hardware Simulator (2.5) - C:\Users\nimit\OneDrive\Desktop\nand2tetris\nand2tetris\projects\03\al\SevenSegmentDisplay.hdl

File View Run Help

Chip Name: SevenSegmentDisplay Time: 0

Input pins		Output pins	
Name	Value	Name	Value
in[4]	0110	a	0
		b	1
		c	0
		d	0
		e	0
		f	1
		g	1

HDL

```
CHIP SevenSegmentDisplay {
    IN in[4];
    OUT a,b,c,d,e,f,g;

    PARTS:
        Mux16n = in[0],out = a0;
        Mux16n = in[1],out = a1;
        Mux16n = in[2],out = a2;
        Mux16n = in[3],out = a3;

    //output for a
    And(a2,b=a0,out=a1);
    And(a2,b=a1,out=a2);
    And(a2,b=a2,out=a3);
    And(a2,b=a3,out=a4);
}
```

Internal pins

Name	Value
a0	0
a1	0
a2	0
a3	0
a4	0
a5	0
a6	0
a7	0
a8	0
a9	0
a10	0
a11	0
a12	0
a13	0
a14	0
a15	0

Hardware Simulator (2.5) - C:\Users\nimit\OneDrive\Desktop\nand2tetris\nand2tetris\projects\03\al\SevenSegmentDisplay.hdl

File View Run Help

Chip Name: SevenSegmentDisplay Time: 0

Input pins		Output pins	
Name	Value	Name	Value
in[4]	0110	a	0
		b	1
		c	0
		d	0
		e	0
		f	1
		g	1

HDL

```
CHIP SevenSegmentDisplay {
    IN in[4];
    OUT a,b,c,d,e,f,g;

    PARTS:
        Mux16n = in[0],out = a0;
        Mux16n = in[1],out = a1;
        Mux16n = in[2],out = a2;
        Mux16n = in[3],out = a3;

    //output for a
    And(a2,b=a0,out=a1);
    And(a2,b=a1,out=a2);
    And(a2,b=a2,out=a3);
    And(a2,b=a3,out=a4);
}
```

Internal pins

Name	Value
a0	0
a1	0
a2	1
a3	0
a4	0
a5	0
a6	0
a7	0
a8	0
a9	0
a10	0
a11	0
a12	0
a13	0
a14	0
a15	0

Hardware Simulator (2.5) - C:\Users\nimit\OneDrive\Desktop\nand2tetris\nand2tetris\projects\03\al\SevenSegmentDisplay.hdl

File View Run Help

Chip Name: SevenSegmentDisplay Time: 0

Input pins		Output pins	
Name	Value	Name	Value
in[4]	0110	a	0
		b	1
		c	0
		d	0
		e	0
		f	1
		g	1

HDL

```
CHIP SevenSegmentDisplay {
    IN in[4];
    OUT a,b,c,d,e,f,g;

    PARTS:
        Mux16n = in[0],out = a0;
        Mux16n = in[1],out = a1;
        Mux16n = in[2],out = a2;
        Mux16n = in[3],out = a3;

    //output for a
    And(a2,b=a0,out=a1);
    And(a2,b=a1,out=a2);
    And(a2,b=a2,out=a3);
    And(a2,b=a3,out=a4);
}
```

Internal pins

Name	Value
a0	0
a1	0
a2	1
a3	0
a4	0
a5	0
a6	0
a7	0
a8	0
a9	0
a10	0
a11	0
a12	0
a13	0
a14	0
a15	0

**THANK YOU**